

**DEPARTMENT OF COMPUTER & SOFTWARE ENGINEERING
COLLEGE OF E&ME, NUST, RAWALPINDI**



Computer System Architecture

**Pipelined Processor
Semester Project Report**

SUBMITTED TO:

Asst Prof Shahid Ismail / Engr. Usama Shoukat

SUBMITTED BY:

**Aleeza Rizwan
Reg# 456143**

**Ibrahim Abdullah
Reg# 454188**

**Aina Ajmal
Reg# 465903**

**Aameena Qadeer
Reg# 464167**

CE 45 A

Submission Date: 1st January, 2025.

Objective

The objective of this project is to design and implement a pipelined processor capable of efficiently managing instruction hazards through stalling and data forwarding techniques. The processor will be designed to demonstrate three distinct operational modes: stall-only design, forwarding-based design, and a combined stall + forwarding design. The implementation will use an instruction set architecture (ISA) such as MIPS, RISC-V, or ARM, selected for its suitability in demonstrating these concepts. The design will be verified through simulation to ensure correct functionality and performance under various scenarios. Additionally, the project aims to provide a detailed hardware structure (RTL), a fully functional Verilog implementation with a testbench, and an example instruction set to showcase the processor's capabilities. This work will contribute to a deeper understanding of pipelined processor design, hazard mitigation, and efficient instruction execution.

Introduction

Pipelining is a widely used technique in computer architecture aimed at improving instruction throughput by overlapping the execution of multiple instructions. However, instruction dependencies often introduce hazards that can disrupt the smooth flow of the pipeline. These hazards are broadly classified into data hazards, control hazards, and structural hazards. To address these challenges, techniques such as stalling and data forwarding (bypassing) are employed. Stalling pauses the pipeline until dependencies are resolved, while forwarding allows intermediate results to be directly passed to dependent instructions, reducing unnecessary delays. This project focuses on designing a pipelined processor capable of demonstrating three distinct operational modes: stall-only design, forwarding-based design, and stall + forwarding-based design.

Features

- **Pipeline Stages:** The instruction execution process will be broken down into stages: instruction fetch, decode, execute, memory access (if needed), and write-back of results.
- **Instruction Set Support:** The processor will support a specific set of commonly used instructions, including basic operations like addition, data movement, and conditional decisions.
- **Pipeline Hazards Handling:** Techniques will be implemented to handle pipeline hazards, such as instruction conflicts or branches that alter the execution flow, to ensure smooth operation.
- **Branch Prediction:** Conditional branch outcomes will be predicted to keep the pipeline running smoothly, reducing delays by processing instructions ahead of time.
- **Data Forwarding:** Shortcuts will be established to pass data directly between pipeline stages, reducing delays associated with traditional data movement through the pipeline.
- **Memory Access:** The processor will efficiently read from and write to the memory subsystem as needed during execution.
- **Simulation and Testing:** Extensive testing will be conducted to ensure the processor works correctly under various scenarios and to identify potential issues before advancing.
- **Performance Evaluation:** The processor's performance will be evaluated by measuring instruction throughput, task completion speed, and resource efficiency.


```

output [4:0] regMuxOut,
output [4:0] regMuxOutEX,
output [4:0] regMuxOutMEM,
output [31:0] branchAdderOUT,
output [31:0] branchAddress,
output ZeroStored,
output [31:0] AluvalueStoredEX,
output [31:0] AluValueStoredMEM,
output PCSRC,
output [31:0] readValueStored,
output [31:0] MemRegMUXOut,

//Control Outputs
output memtoregID,
output memtoregEX,
output memtoregWB,
output memwriteID,
output memwriteEX,
output branchID,
output branchEX,
output [2:0] aluControlID,
output aluSrcID,
output regdstID,
output regwriteID,
output regwriteEX,
output regwriteWB,
output memReadID,
output memReadEX,

//Forwarding
output [1:0] ForwardA,
output [1:0] ForwardB,
output [31:0] ForwardAluSRCA,
output [31:0] ForwardAluSRCB,

//Hazard
output Hazard,

//Branch Hazard
output branchDetected

);

//Wires
//ALU
wire [31:0] alu_result;
wire alu_zero;

```

```

//Reg file
wire [31:0] reg_rsData;
wire [31:0] reg_rtData;
//Inst mem
wire [31:0] inst_instruct;
//Data mem
wire [31:0] data_rd;
//PC
wire [31:0] pc_pcout;
//Decoder
wire [4:0] int_shamt;
wire [5:0] int_func;
wire [15:0] int_immed;
wire [25:0] int_target;
wire [4:0] int_rs;
wire [4:0] int_rt;
wire [4:0] int_rd;
wire [5:0] int_opcode;
wire [31:0] int_shiftl16;
//Control Signal
wire int_memtoreg;
wire int_memwrite;
wire int_branch;
wire [2:0] int_aluControl;
wire int_aluSrc;
wire int_regdst;
wire int_regwrite;
wire [31:0] int_signExtend;
wire pc_jump;
wire int_memRead;
//ALU Src
wire [31:0] int_aluSrcSelect;
//ResultSelect
wire [31:0] int_resultSel;
//RegSelect
wire [4:0] int_rsOrd;
wire Hazardrst_int;

//Calling MUX
mux1 mux1_int (
                                .branch(PCSRC),
                                .pcvalue(pc_pcout),
                                .branchvalue(branchAddress),
                                .muxOut(mux1Out)
                                );

```

```

//Calling Program Counter
pc pc_int (
    .clk(clk),
    .rst(rst),
    .pcOut(pc_pcout),
    .hazard(Hazard),
    .pcIn(mux1Out),
    .pcprev(pcStoredIF)
);

//Instantiating Instruction memory
inst_mem instmem_int (
    .address(pc_pcout),
    .instruction(inst_instruct)
);

//Calling the Fetch/Decode pipelined module
IFID IFID_int (
    .clk(clk),
    .pcvalue(pc_pcout),
    .pcStored(pcStoredIF),
    .instructionvalue(inst_instruct),
    .instructionStored(instructionStored)
);

//Calling Decoder
Decoder decode_int (
    .instruct(instructionStored),
    .opcode(int_opcode),
    .rs(int_rs),
    .rt(int_rt),
    .rd(int_rd),
    .shamt(int_shamt),
    .func(int_func),
    .immed(int_immed),
    .signExtend(int_signExtend),
    .target(int_target),
    .slby16(int_shiftl16)
);

//Instantiating the registers from reg file
reg_file regfile_int (
    .rs(int_rs),
    .rt(int_rt),
    .rd(regMuxOutMEM),
    .rst(rst),

```

```

        .write(regwriteWB),
        .rsData(reg_rsData),
        .rtData(reg_rtData),
        .mem_write(MemRegMUXOut)
    );

//Calling Decode/Execute pipeline module
IDEX IDEX_int (
    .clk(clk),
    .pcvalue(pcStoredIF),
    .pcvalueStored(pcStoredID),
    .rsDt(reg_rsData),
    .rsDtStored(rsDTStored),
    .rtDt(reg_rtData),
    .rtDtStored(rtDTStoredID),
    .signEx(int_signExtend),
    .signExStored(signexStored),
    .rtval(int_rt),
    .rtvalStored(rtValStored),
    .rdval(int_rd),
    .rdvalStored(rdValStored),
    .memtoreg(int_memtoreg),
    .memtoregStored(memtoregID),
    .memwrite(int_memwrite),
    .memwriteStored(memwriteID),
    .branch(int_branch),
    .branchStored(branchID),
    .aluControl(int_aluControl),
    .aluControlStored(aluControlID),
    .aluSrc(int_aluSrc),
    .aluSrcStored(aluSrcID),
    .regdst(int_regdst),
    .regdstStored(regdstID),
    .regwrite(int_regwrite),
    .regwriteStored(regwriteID),
    .rsval(int_rs),
    .rsvalStored(rsValStored),
    .memRead(int_memRead),
    .memReadStored(memReadID),
    .hazard(Hazard),
    .branchDet(branchDetected)
);

//Instantiating the destination register
dstRegMux dstRegMux_int (

```



```

        .regdst(regdstID),
        .rt(rtValStored),
        .rd(rdValStored),
        .regmuxOut(regMuxOut)
    );

//Calling BranchAdderModule

branchAdder branchAdder_int (
    .pc(pcStoredID),
    .signEx(signexStored),
    .branchAdderOut(branchAdderOUT)
);

//Calling the Control Unit
ControlUnit control_int (
    .opcode(int_opcode),
    .func(int_func),
    .memtoreg(int_memtoreg),
    .memwrite(int_memwrite),
    .branch(int_branch),
    .aluControl(int_aluControl),
    .aluSrc(int_aluSrc),
    .regdst(int_regdst),
    .regwrite(int_regwrite),
    .jump(pc_jump),
    .memRead(int_memRead)
);

//Calling Module for the Control Signal of ALU
AluSrc src_int (
    .Rt(rtDTStoredID),
    .signExtend(int_signExtend),
    .alusrc(aluSrcID),
    .result(int_aluSrcSelect)
);

//Calling ALU
Alu Alu_int (
    .srcA(ForwardAluSRCA),
    .srcB(ForwardAluSRCB),
    .opcode(aluControlID),
    .signExtend(int_signExtend),
    .zero(alu_zero),
    .result(alu_result)
);

//Forwarding unit

```

```

ForwardingUnit ForwardingUnit_int (
    .EXregwrite(regwriteEX),
    .WBregwrite(regwriteWB),
    .curRs(rsValStored),
    .curRt(rtValStored),
    .exRd(regMuxOutEX),
    .wbRd(regMuxOutMEM),
    .forwardA(ForwardA),
    .forwardB(ForwardB)
);

ForwardMux1 ForwardMux1_int (
    .forwardA(ForwardA),
    .curRSdt(rsDTStored),
    .EXRSdt(AluvalueStoredEX),
    .MEMRSdt(MemRegMUXOut),
    .aluSRCA(ForwardAluSRCA)
);

ForwardMux2 ForwardMux2_int (
    .forwardB(ForwardB),
    .curRTdt(int_aluSrcSelect),
    .EXRTdt(AluvalueStoredEX),
    .MEMRTdt(MemRegMUXOut),
    .aluSRCB(ForwardAluSRCB)
);

//Calling Module for the Detection of Hazards
HazardDetection HazardDetection_int (
    .exMemRead(memReadEX),
    .curRs(int_rs),
    .curRt(int_rt),
    .exRd(rdValStored),
    .hazard(Hazard)
);

//Branch Hazards
BranchHazard BranchHazard_int (
    .branch(PCSRC),
    .branchDet(branchDetected)
);

//Calling the Execute/Memory Pipeline module
EXMEM EXMEM_int (
    .clk(clk),
    .pcvalue(branchAdderOUT),
    .pcvalueStored(branchAddress),
    .zero(alu_zero),

```

```

        .zeroStored(ZeroStored),
        .aluvalue(alu_result),
        .aluvalueStored(AluvalueStoredEX),
        .rtDt(rtDTStoredID),
        .rtDtStored(rtDtStoredEX),
        .rsrd(regMuxOut),
        .rsrdStored(regMuxOutEX),
        .memtoreg(memtoregID),
        .memtoregStored(memtoregEX),
        .memwrite(memwriteID),
        .memwriteStored(memwriteEX),
        .branch(branchID),
        .branchStored(branchEX),
        .regwrite(regwriteID),
        .regwriteStored(regwriteEX),
        .memRead(memReadID),
        .memReadStored(memReadEX),
        .branchDet(branchDetected)

    );

//Module for Checking Branch Conditions
branchCondit branchCondit_int (

    .branch(branchEX),
    .zero(ZeroStored),
    .pcSRC(PCSRC)

);

//Instantiating Values from Memory by Calling DataMem
datamemory datamemory_int (

    .writeEn(memwriteEX),
    .writedata(rtDtStoredEX),
    .a(AluvalueStoredEX),
    .rd(data_rd),
    .memRead(memReadEX)

);

//Calling Memory/WriteBack Pipeline module
MEMWB MEMWB_int (

    .clk(clk),
    .readvalue(data_rd),
    .readvalueStored(readValueStored),
    .aluvalue(AluvalueStoredEX),
    .aluvalueStored(AluValueStoredMEM),
    .rsrd(regMuxOutEX),
    .rsrdStored(regMuxOutMEM),
    .memtoreg(memtoregEX),

```

```

        .memtoregStored(memtoregWB),
        .regwrite(regwriteEX),
        .regwriteStored(regwriteWB)
    );

    //Instantiating memTOregMux Module
    memTOregMux memTOregMux_int (
        .memtoreg(memtoregWB),
        .readval(readValueStored),
        .aluval(AluValueStoredMEM),
        .MemRegOut(MemRegMUXOut)
    );

endmodule

```

Other Modules

```

module mux1(
    input wire branch,        // Branch control signal
    input wire [31:0] pcvalue, // Value from the PC
    input wire [31:0] branchvalue, // Branch target address
    output wire [31:0] muxOut  // Output of the multiplexer
);

    // Multiplexer logic: if branch is true, output branch value, otherwise output pcvalue
    assign muxOut = (branch) ? branchvalue : pcvalue;

endmodule

module pc #(parameter N=32)
(
    input clk,
    input rst,
    output reg [N-1:0] pcOut,
    input hazard,
    input [N-1:0] pcIn,
    input [31:0] pcprev
);

    always @(posedge clk or posedge rst)
    begin
        if (rst)
            begin
                pcOut <= {N{1'b0}}; // Reset pcOut to 0
            end
        else begin

```

```

    if (hazard) begin
        pcOut <= pcprev; // Retain previous PC value during hazard
    end
    else begin
        if (pcIn == 31) begin
            pcOut <= 0; // Reset to 0 when pcIn reaches 31
        end
        else begin
            pcOut <= pcIn + 1; // Increment PC
        end
    end
end
end
end

endmodule

module inst_mem #(parameter N=32, D=32)
(
    input [N-1:0] address,
    output reg [N-1:0] instruction
);

    reg [N-1:0] memory [D-1:0];

    initial begin
        // Initialize memory with instructions
        memory[0] = 32'b000000_00000_01010_00001_00000_000000; // lw $t2, 0($t0)
        memory[1] = 32'b000001_00011_00001_00000_00000_000100; // sw $t4, 0($t0)
        memory[2] = 32'b000100_00011_00001_00000_00000_100101; // or $t3,$t4, $t1
        memory[3] = 32'b000100_01011_00001_00000_00000_100010; // sub $t3,$t2, $t1
        memory[4] = 32'b000100_00010_00011_00000_00000_100101; // or $t4, $t2, $t3
        memory[5] = 32'b000000_00011_00001_00000_00000_000100; // lw $t4, 0($t0)
        memory[6] = 32'b000010_00110_00101_00000_00000_000001; // beq
        memory[7] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1, $t0
        memory[8] = 32'b000100_01010_01011_01001_00000_100000; // add $t2,$t2, $t3
        memory[9] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4, $t1
        memory[10] = 32'b000100_00001_01011_01010_00000_100000; // add $t2,$t1,$t3
        memory[11] = 32'b000011_00000_00000_00000_00000_000010; // jump
        memory[12] = 32'b000001_00000_01010_00001_00000_000000; // sw $t2, 0($t0)
        memory[13] = 32'b000000_00000_01011_00001_00000_000000; // lw $t3, 0($t0)
        memory[14] = 32'b000000_00000_01010_00001_00000_000000; // lw $t2, 0($t0)
        memory[15] = 32'b000100_01011_00001_00000_00000_100010; // sub $t3,$t2,$t1
        memory[16] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
        memory[17] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
    end
end

```

```

memory[18] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[19] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[20] = 32'b000100_00010_00001_00000_00000_100100; // and $t2,$t1,$t0
memory[21] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[22] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[23] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[24] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[25] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[26] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[27] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[28] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[29] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
memory[30] = 32'b000100_00010_00001_00000_00000_000001; // add $t2,$t1,$t0
memory[31] = 32'b000100_00011_00001_00000_00000_000001; // add $t3,$t4,$t1
end

always @* begin
    // Ensure the address is divided by 4 to index the instruction memory properly
    instruction = memory[address >> 2];
end
endmodule

module IFID
(
    input clk,
    input rst,          // Reset signal to initialize registers
    input [31:0] pcvalue, // Input PC value
    output reg [31:0] pcStored, // Stored PC value
    input [31:0] instructionvalue, // Input instruction value
    output reg [31:0] instructionStored // Stored instruction value
);

// Always block triggered on positive edge of the clock or reset
always @(posedge clk or posedge rst) begin
    if (rst) begin
        // Initialize the registers to 0 on reset
        pcStored <= 32'b0;
        instructionStored <= 32'b0;
    end else begin
        // Store the current PC and instruction values on the rising edge of clock
        pcStored <= pcvalue;
        instructionStored <= instructionvalue;
    end
end
end

```

```

endmodule

module Decoder(
    input [31:0] instruct,
    output reg [5:0] opcode,
    output reg [4:0] rs,
    output reg [4:0] rt,
    output reg [4:0] rd,
    output reg [4:0] shamt,
    output reg [5:0] func,
    output reg [15:0] immed,
    output reg [31:0] signExtend,
    output reg [25:0] target,
    output reg [31:0] slby16
);
    always@(*)
    begin
        opcode<=instruct[31:26];
        rs<=instruct[25:21];
        rt<=instruct[20:16];
        rd<=instruct[15:11];
        shamt<=instruct[10:6];
        func<=instruct[5:0];
        immed<=instruct[15:0];
        slby16<=immed << 16;
        signExtend<={ {16{immed[15]}}, immed };
        target<=instruct[25:0];
    end
endmodule

module reg_file #(parameter N=32,D=32)(
    input [4:0] rs,
    input [4:0] rt,
    input [4:0] rd,
    input rst,
    input write,
    output reg [N-1:0] rsData,
    output reg [N-1:0] rtData,
    input [N-1:0] mem_write
);
    reg [N-1:0]memory [D-1:0];
    initial
    begin
        memory[0]=32'd550;
    end
endmodule

```

```

memory[1]=32'd600;
memory[2]=32'd550;
memory[3]=32'd600;
memory[4]=32'd432;
memory[5]=32'd543;
memory[6]=32'd800;
memory[7]=32'd210;
memory[8]=32'd140;
memory[9]=32'd940;
memory[10]=32'd1320;
memory[11]=32'd160;
memory[12]=32'd830;
memory[13]=32'd400;
memory[14]=32'd340;
memory[15]=32'd270;
memory[16]=32'd550;
memory[17]=32'd1000;
memory[18]=32'd220;
end
always@(*)
begin
rsData=memory[rs];
rtData=memory[rt];
end
//assign rsData=memory[rs];
//assign rtData=memory[rt];
always@(*)
begin
if(write)
memory[rd]<=mem_write;
end

endmodule

module IDEX(
input clk,
input rst,           // Reset signal to initialize registers
input [31:0] pcvalue, // Input PC value
output reg [31:0] pcvalueStored, // Stored PC value
input [31:0] rsDt,    // Input RS data value
output reg [31:0] rsDtStored, // Stored RS data
input [31:0] rtDt,    // Input RT data value
output reg [31:0] rtDtStored, // Stored RT data
input [31:0] signEx,  // Input sign-extended value
output reg [31:0] signExStored, // Stored sign-extended value
input [4:0] rtval,    // Input RT register value

```



```

output reg [4:0] rtvalStored, // Stored RT register value
input [4:0] rdval, // Input RD register value
output reg [4:0] rdvalStored, // Stored RD register value
input memtoreg, // Control signal for mem-to-reg
output reg memtoregStored, // Stored mem-to-reg control signal
input memwrite, // Control signal for memory write
output reg memwriteStored, // Stored memory write control signal
input branch, // Control signal for branching
output reg branchStored, // Stored branch control signal
input [2:0] aluControl, // ALU control signal
output reg [2:0] aluControlStored, // Stored ALU control signal
input aluSrc, // ALU source control signal
output reg aluSrcStored, // Stored ALU source control signal
input regdst, // Register destination control signal
output reg regdstStored, // Stored regdst control signal
input regwrite, // Register write control signal
output reg regwriteStored, // Stored register write control signal
input [4:0] rsval, // RS value (for forwarding)
output reg [4:0] rsvalStored, // Stored RS value
input memRead, // Memory read control signal
output reg memReadStored, // Stored memory read control signal
input hazard, // Hazard detection signal
input branchDet // Branch detection signal
);

// Always block triggered on positive edge of the clock or reset
always @(posedge clk or posedge rst)
begin
    if (rst) begin
        // Initialize all registers to 0 on reset
        pcvalueStored <= 32'b0;
        rsDtStored <= 32'b0;
        rtDtStored <= 32'b0;
        signExStored <= 32'b0;
        rsvalStored <= 5'b0;
        rtvalStored <= 5'b0;
        rdvalStored <= 5'b0;
        memtoregStored <= 0;
        memwriteStored <= 0;
        branchStored <= 0;
        aluControlStored <= 3'b0;
        aluSrcStored <= 0;
        regdstStored <= 0;
        regwriteStored <= 0;
        memReadStored <= 0;
    end
end

```

```

else if (hazard || branchDet) begin
    // Disable memory write and register write when hazard or branch detected
    memwriteStored <= 0;
    regwriteStored <= 0;
end

else begin
    // Store input values when no hazard or branch is detected
    pcvalueStored <= pcvalue;
    rsDtStored <= rsDt;
    rtDtStored <= rtDt;
    signExStored <= signEx;
    rsvalStored <= rsval;
    rtvalStored <= rtval;
    rdvalStored <= rdval;
    memtoregStored <= memtoreg;
    memwriteStored <= memwrite;
    branchStored <= branch;
    aluControlStored <= aluControl;
    aluSrcStored <= aluSrc;
    regdstStored <= regdst;
    regwriteStored <= regwrite;
    memReadStored <= memRead;
end
end

endmodule

module dstRegMux
(
    input wire regdst,
    input wire [4:0] rt,
    input wire [4:0] rd,
    output wire [4:0] regmuxOut
);
    assign regmuxOut = regdst ? rd : rt;
endmodule

module branchAdder
(
    input [31:0] pc,
    input [31:0] signEx,
    output reg [31:0] branchAdderOut
);

```

```

    reg [31:0] branch;
    reg [4:0] branchH;
    always @(*)
    begin
        branch<=signEx <<2;
        branchH<=branch[4:0];
        branchAdderOut=pc + branchH;
    end

endmodule

module ControlUnit
(
    input [5:0] opcode,
    input [5:0] func,
    output reg memtoreg,
    output reg memwrite,
    output reg branch,
    output reg [2:0] aluControl,
    output reg aluSrc,
    output reg regdst,
    output reg regwrite,
    output reg jump,
    output reg memRead
);

    always@(opcode or func)
    begin
        case(opcode)
            //xori
            6'b001001:
                begin
                    aluControl<=3'b111;
                    memtoreg<=0;
                    branch<=1'b0;
                    aluSrc<=1'b1;
                    regdst<=1'b0;
                    regwrite<=1'b1;
                    jump<=1'b0;
                    memRead<=1'b0;
                end
            //slti
            6'b001000:
                begin
                    aluControl<=3'b101;
                    memtoreg<=0;

```

```

        branch<=1'b0;
        aluSrc<=1'b1;
        regdst<=1'b1;
        regwrite<=1'b1;
        jump<=1'b0;
        memRead<=1'b0;
    end
//slt
6'b000111:
    begin
        aluControl<=3'b111;
        memtoreg<=0;
        branch<=1'b0;
        aluSrc<=1'b0;
        regdst<=1'b1;
        regwrite<=1'b1;
        jump<=1'b0;
        memRead<=1'b0;
    end
//and
6'b000110:
    begin
        aluControl<=3'b011;
        memtoreg<=0;
        branch<=1'b0;
        aluSrc<=1'b1;
        regdst<=1'b0;
        regwrite<=1'b1;
        jump<=1'b0;
        memRead<=1'b0;
    end
//lui
6'b000101:
    begin
        aluControl<=3'b010;
        memtoreg<=2'b10;
        branch<=1'b0;
        aluSrc<=1'b0;
        regdst<=1'b0;
        regwrite<=1'b1;
        jump<=1'b0;
        memRead<=1'b0;
    end
//lw
6'b000000:
    begin

```

```

        aluControl<=3'b010;
        memtoreg<=1'b1;
        branch<=1'b0;
        aluSrc<=1'b1;
        memwrite<=1'b0;
        regdst<=1'b1;
        regwrite<=1'b0;
        jump<=1'b0;
        memRead<=1'b1;
    end
//sw
6'b000001:
    begin
        aluControl<=3'b010;
        memtoreg<=1'b0;
        memwrite<=1'b1;
        branch<=1'b0;
        aluSrc<=1'b1;
        regdst<=1'b0;
        regwrite<=1'b0;
        jump<=1'b0;
        memRead<=1'b0;
    end
//beq
6'b000010:
    begin
        aluControl<=3'b110;
        memtoreg<=1'b0;
        memwrite<=1'b0;
        branch<=1'b1;
        aluSrc<=1'b0;
        regdst<=1'b0;
        regwrite<=1'b0;
        jump<=1'b0;
        memRead<=1'b0;
    end
//jump
6'b000011:
    begin
        aluControl<=3'b010;
        memtoreg<=2'b00;
        memwrite<=1'b1;
        branch<=1'b0;
        aluSrc<=1'b0;
        regdst<=1'b1;
        regwrite<=1'b1;
    end

```

```

        jump<=1'b1;
        memRead<=1'b0;
    end
6'b000100:
    case(func)
        //add
        6'b100000:
            begin
                aluControl<=3'b010;
                memtoreg<=2'b00;
                memwrite<=1'b1;
                branch<=1'b0;
                aluSrc<=1'b0;
                regdst<=1'b1;
                regwrite<=1'b1;
                jump<=1'b0;
                memRead<=1'b0;
            end
        //sub
        6'b100010:
            begin
                aluControl<=3'b110;
                memtoreg<=2'b00;
                memwrite<=1'b1;
                branch<=1'b0;
                aluSrc<=1'b0;
                regdst<=1'b1;
                regwrite<=1'b1;
                jump<=1'b0;
                memRead<=1'b0;
            end
        //and
        6'b100100:
            begin
                aluControl<=3'b011;
                memtoreg<=2'b00;
                memwrite<=1'b1;
                branch<=1'b0;
                aluSrc<=1'b0;
                regdst<=1'b1;
                regwrite<=1'b1;
                jump<=1'b0;
                memRead<=1'b0;
            end
        //or
        6'b100101:

```

```

        begin
            aluControl<=3'b001;
            memtoreg<=2'b00;
            memwrite<=1'b1;
            branch<=1'b0;
            aluSrc<=1'b0;
            regdst<=1'b1;
            regwrite<=1'b1;
            jump<=1'b0;
            memRead<=1'b0;
        end
        //set on less than
        6'b101010:
        begin
            aluControl<=3'b111;
            memtoreg<=2'b00;
            memwrite<=1'b1;
            branch<=1'b0;
            aluSrc<=1'b0;
            regdst<=1'b1;
            regwrite<=1'b1;
            jump<=1'b0;
            memRead<=1'b0;
        end
        default:
        begin
            aluControl<=3'b000;
            memtoreg<=2'b00;
            memwrite<=1'b0;
            branch<=1'b0;
            aluSrc<=1'b0;
            regdst<=1'b0;
            regwrite<=1'b0;
            jump<=1'b0;
            memRead<=1'b0;
        end
    endcase
default:
    begin
        aluControl<=3'b000;
        memtoreg<=2'b00;
        memwrite<=1'b0;
        branch<=1'b0;
        aluSrc<=1'b0;
        regdst<=1'b0;
        regwrite<=1'b0;
    end

```

```

                                jump<=1'b0;
                                memRead<=1'b0;
                                end
                                endcase
                                end

                                endmodule

                                module AluSrc
                                (
                                    input [31:0] Rt,
                                    input [31:0] signExtend,
                                    input alusrc,
                                    output reg [31:0] result
                                );
                                    always@(alusrc or Rt or signExtend)
                                    begin
                                        if(alusrc)
                                            result<=signExtend;
                                        else
                                            result<=Rt;
                                        end
                                    end

                                endmodule

                                module Alu
                                (
                                    input [31:0] srcA,
                                    input [31:0] srcB,
                                    input [2:0] opcode,
                                    input [31:0] signExtend,
                                    output reg zero,
                                    output reg [31:0] result,
                                    output reg [31:0] HI_reg,
                                    output reg [31:0] LO_reg
                                );

                                    reg [31:0] evenCheck;
                                    wire [31:0] divi;
                                    assign divi=32'd2;
                                    always @(*) begin
                                        case (opcode)
                                            3'b010: result = srcA + srcB;
                                            3'b110: result = srcA - srcB;
                                            3'b010: result = srcA + srcB;
                                            3'b110: result = srcA - srcB;
                                        endcase
                                    end
                                endmodule

```



```

//3'b000: result = srcA & srcB;
3'b000: begin
    result=srcA * srcB;
    {HI_reg,LO_reg}=result;
end
3'b001: result = srcA | srcB;
//3'b100: result = srcA ^ srcB;
//3'b111: result = srcA < srcB? 1:0;
3'b111: begin    /// xori instruction
    evenCheck = srcA ^ signExtend;
    result= evenCheck%divi==0? evenCheck: srcB;
end
3'b101: result = srcA < signExtend? 1:0;
3'b011: result = srcA & srcB;
default: result = srcA;
endcase

if (result == 32'd0)
    zero <= 1'b1;
else
    zero <= 1'b0;
end

endmodule

module ForwardingUnit
(
    input EXregwrite,
    input WBregwrite,
    input [4:0] curRs,
    input [4:0] curRt,
    input [4:0] exRd,
    input [4:0] wbRd,
    output [1:0] forwardA,
    output [1:0] forwardB
);
    assign forwardA = (EXregwrite && curRs==exRd) ? 2'b01:
        (WBregwrite && curRs==wbRd) ? 2'b10:
        2'b00;

    assign forward = (EXregwrite && curRt==exRd) ? 2'b01:
        (WBregwrite && curRt==wbRd) ? 2'b10:
        2'b00;
endmodule

module ForwardMux1

```

```

(
    input [1:0] forwardA,
    input [31:0] curRSdt,
    input [31:0] EXRSdt,
    input [31:0] MEMRSdt,
    output [31:0] aluSRCA
);
    assign aluSRCA = (forwardA==2'b01) ? EXRSdt:
                     (forwardA==2'b10) ? MEMRSdt : curRSdt;

endmodule

module ForwardMux2
(
    input [1:0] forwardB,    // Forwarding control signal
    input [31:0] curRTdt,    // RT value from the current instruction
    input [31:0] EXRTdt,    // RT value from EX stage
    input [31:0] MEMRTdt,    // RT value from MEM stage
    output [31:0] aluSRCB    // Second operand for ALU
);

    // Forwarding logic
    assign aluSRCB = (forwardB == 2'b01) ? EXRTdt : // Forward from EX stage
                     (forwardB == 2'b10) ? MEMRTdt : // Forward from MEM stage
                     curRTdt;                       // Use current RT value

endmodule

module HazardDetection
(
    input exMemRead,
    input [4:0] curRs,
    input [4:0] curRt,
    input [4:0] exRd,
    output reg hazard
);
    always @(*)
    begin
        hazard<=1'b0;
        hazard <=(exMemRead && ((curRs == exRd) || (curRt == exRd))) ? 1'b1: 1'b0;
    end
endmodule

module BranchHazard
(
    input branch,

```

```

        output reg branchDet
    );
    always@(*)
    begin
        if(branch)
            branchDet<=1'b1;
        else
            branchDet<=1'b0;
        end

endmodule

module EXMEM
(
    input clk,
    input [31:0] pcvalue,
    output reg [31:0] pcvalueStored,
    input zero,
    output reg zeroStored,
    input [31:0] aluvalue,
    output reg [31:0] aluvalueStored,
    input [31:0] rtDt,
    output reg [31:0] rtDtStored,
    input [4:0] rsrd,
    output reg [4:0] rsrdStored,
    input memtoreg,
    output reg memtoregStored,
    input memwrite,
    output reg memwriteStored,
    input branch,
    output reg branchStored,
    input regwrite,
    output reg regwriteStored,
    input memRead,
    output reg memReadStored,
    input branchDet
);
    always @(posedge clk)
    begin
        if(branchDet)
        begin
            memwriteStored<=1'b0;
            regwriteStored<=1'b0;
            zeroStored <= 1'b0;
        end
        else

```

```

begin
    pcvalueStored <= pcvalue;
    zeroStored <= zero;
    aluvalueStored <= aluvalue;
    rtDtStored <= rtDt;
    rsrdStored <= rsrd;
    memtoregStored <= memtoreg;
    memwriteStored <= memwrite;
    branchStored <= branch;
    regwriteStored <= regwrite;
    memReadStored <= memRead;
end
end
endmodule

module branchCondit
(
    input wire branch,
    input wire zero,
    output reg pcSRC
);
    always @(*)
    begin
        pcSRC <= (branch && zero) ? 1 : 0;
    end
endmodule

module datamemory
(
    input wire writeEn,
    input wire [31:0] writedata,
    input wire [31:0] a,
    output reg [31:0] rd,
    input wire memRead
);

    reg [31:0] memory [0:31]; // Define a memory array of 32 elements

    // Initialize memory with some values
    initial begin
        memory[0] = 32'd5;
        memory[1] = 32'd50;
        memory[2] = 32'd55;
        memory[3] = 32'd6;
        memory[4] = 32'd4;
        memory[5] = 32'd43;
    end
endmodule

```

```

memory[6] = 32'd80;
memory[7] = 32'd21;
memory[8] = 32'd40;
memory[9] = 32'd90;
memory[10] = 32'd20;
memory[11] = 32'd10;
memory[12] = 32'd30;
memory[13] = 32'd40;
memory[14] = 32'd39;
memory[15] = 32'd27;
memory[16] = 32'd52;
memory[17] = 32'd1000;
memory[18] = 32'd22;
memory[19] = 32'd560;
memory[20] = 32'd420;
memory[21] = 32'd690;
memory[22] = 32'd2;
memory[23] = 32'd1;
memory[24] = 32'd3;
memory[25] = 32'd7;
memory[26] = 32'd4;
memory[27] = 32'd16;
memory[28] = 32'd72;
memory[29] = 32'd13;
memory[30] = 32'd60;
memory[31] = 32'd8;
end

// Memory write operation (synchronous)
always @(*) begin
    if (writeEn) begin
        memory[a[4:0]] <= writedata; // Use only lower 5 bits of 'a' for addressing
    end
end

// Memory read operation (combinational)
always @(*) begin
    if (memRead) begin
        rd = memory[a[4:0]]; // Use only lower 5 bits of 'a' for addressing
    end else begin
        rd = 32'b0; // Default value when memRead is not asserted
    end
end

endmodule

```

```

module MEMWB
(
    input clk,                // Clock signal
    input [31:0] readvalue,    // Data read from memory (Memory read value)
    output reg [31:0] readvalueStored, // Stored memory value for write-back stage
    input [31:0] aluvalue,     // ALU result value (ALU value after execution)
    output reg [31:0] aluvalueStored, // Stored ALU result for write-back stage
    input [4:0] rsrd,         // Register destination (destination register address)
    output reg [4:0] rsrdStored, // Stored destination register address
    input memtoreg,          // Control signal to decide whether to write memory
    data or ALU result
    output reg memtoregStored, // Stored memtoreg control signal for write-back
    input regwrite,          // Control signal to enable/disable register write
    output reg regwriteStored // Stored regwrite control signal for write-back
);

    // Sequential logic to store values at the positive edge of the clock
    always @(posedge clk)
    begin
        // Store the values for the write-back stage (MEM -> WB pipeline stage)
        readvalueStored <= readvalue; // Store memory read value
        aluvalueStored <= aluvalue;   // Store ALU result
        rsrdStored <= rsrd;           // Store destination register address
        memtoregStored <= memtoreg;   // Store memtoreg control signal
        regwriteStored <= regwrite;   // Store regwrite control signal
    end
endmodule

module memTOregMux
(
    input wire memtoreg,
    input wire [31:0] readval,
    input wire [31:0] aluval,
    output wire [31:0] MemRegOut
);
    assign MemRegOut = memtoreg ? readval : aluval;
endmodule

```

Test Bench

```

module MyTestBench;

    // Inputs
    reg clk;
    reg rst;

```

```

// Outputs
wire [31:0] pcStoredIF;
wire [31:0] pcStoredID;
wire [31:0] instructionStored;
wire [31:0] mux1Out;
wire [31:0] rsDTStored;
wire [31:0] rtDTStoredID;
wire [31:0] rtDtStoredEX;
wire [31:0] signexStored;
wire [4:0] rsValStored;
wire [4:0] rtValStored;
wire [4:0] rdValStored;
wire [4:0] regMuxOut;
wire [4:0] regMuxOutEX;
wire [4:0] regMuxOutMEM;
wire [31:0] branchAdderOUT;
wire [31:0] branchAddress;
wire ZeroStored;
wire [31:0] AluvalueStoredEX;
wire [31:0] AluValueStoredMEM;
wire PCSRC;
wire [31:0] readValueStored;
wire [31:0] MemRegMUXOut;
wire memtoregID;
wire memtoregEX;
wire memtoregWB;
wire memwriteID;
wire memwriteEX;
wire branchID;
wire branchEX;
wire [2:0] aluControlID;
wire aluSrcID;
wire regdstID;
wire regwriteID;
wire regwriteEX;
wire regwriteWB;
wire memReadID;
wire memReadEX;
wire [1:0] ForwardA;
wire [1:0] ForwardB;
wire [31:0] ForwardAluSRCA;
wire [31:0] ForwardAluSRCB;
wire Hazard;
wire branchDetected;

```

```

// Instantiate the Unit Under Test (UUT)

```

```


PipelineTop uut (
    .clk(clk),
    .rst(rst),
    .pcStoredIF(pcStoredIF),
    .pcStoredID(pcStoredID),
    .instructionStored(instructionStored),
    .mux1Out(mux1Out),
    .rsDTStored(rsDTStored),
    .rtDTStoredID(rtDTStoredID),
    .rtDtStoredEX(rtDtStoredEX),
    .signexStored(signexStored),
    .rsValStored(rsValStored),
    .rtValStored(rtValStored),
    .rdValStored(rdValStored),
    .regMuxOut(regMuxOut),
    .regMuxOutEX(regMuxOutEX),
    .regMuxOutMEM(regMuxOutMEM),
    .branchAdderOUT(branchAdderOUT),
    .branchAddress(branchAddress),
    .ZeroStored(ZeroStored),
    .AluvalueStoredEX(AluvalueStoredEX),
    .AluValueStoredMEM(AluValueStoredMEM),
    .PCSRC(PCSRC),
    .readValueStored(readValueStored),
    .MemRegMUXOut(MemRegMUXOut),
    .memtoregID(memtoregID),
    .memtoregEX(memtoregEX),
    .memtoregWB(memtoregWB),
    .memwriteID(memwriteID),
    .memwriteEX(memwriteEX),
    .branchID(branchID),
    .branchEX(branchEX),
    .aluControlID(aluControlID),
    .aluSrcID(aluSrcID),
    .regdstID(regdstID),
    .regwriteID(regwriteID),
    .regwriteEX(regwriteEX),
    .regwriteWB(regwriteWB),
    .memReadID(memReadID),
    .memReadEX(memReadEX),
    .ForwardA(ForwardA),
    .ForwardB(ForwardB),
    .ForwardAluSRCA(ForwardAluSRCA),
    .ForwardAluSRCB(ForwardAluSRCB),
    .Hazard(Hazard),
    .branchDetected(branchDetected)

```



```
);  
  
initial begin  
    // Initialize Inputs  
    clk = 0;  
    rst = 1;  
  
    // Wait 100 ns for global reset to finish  
    #100;  
  
    // Deassert reset  
    rst = 0;  
end  
  
// Clock generation process  
always begin  
    #5 clk = ~clk; // Toggle clock every 5 ns (10 ns period)  
end  
  
endmodule
```

RTL Schematic Diagram

 

Conclusion

In conclusion, the design and implementation of our pipelined processor successfully demonstrated effective hazard management through stalling, data forwarding, and a combined stall + forwarding approach. By carefully structuring the processor into key pipeline stages—Fetch, Decode, Execute, Memory Access, and Write-back—we ensured efficient instruction flow while minimizing delays caused by data and control hazards. The integration of hazard detection units and forwarding mechanisms allowed the processor to dynamically resolve dependencies, improving overall performance and reliability.

Through simulation, we validated the functionality and efficiency of our design under real-world conditions. Additionally, the synthesis report provided insights into resource utilization, highlighting areas for potential optimization. This project not only achieved its objectives but also enhanced our understanding of pipelined processor design, hazard management techniques, and digital hardware implementation.